


A decorative graphic on the left side of the slide, consisting of a network of white lines and circles on a blue background, resembling a printed circuit board (PCB) layout or a data network diagram. The lines are of varying thickness and connect to small white circles, creating a complex, branching structure.

02. BASIC ELECTRONICS

M2U1P2

WHAT IS ELECTRICITY?


(ไฟฟ้า)

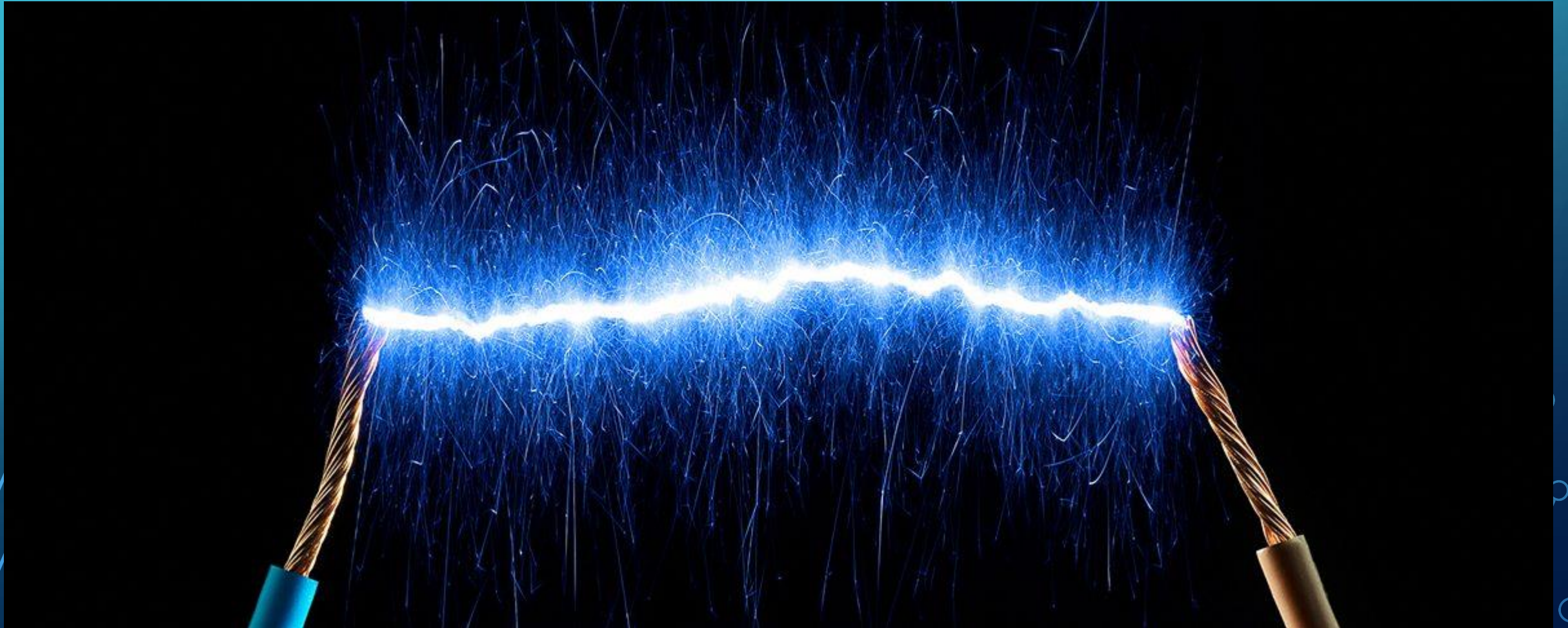

ELECTRICITY (ไฟฟ้า)


- **Electricity** is form of energy which is involved in the movement of electrons and protons, which can be used to convert to other forms of energy such as light, heat, sound, movement....
- Example
 - Light → light bulb
 - Heat → iron
 - Image and sound → TV
 - Movement → motor, something spinning

WHAT ARE ELECTRONS AND PROTONS ?

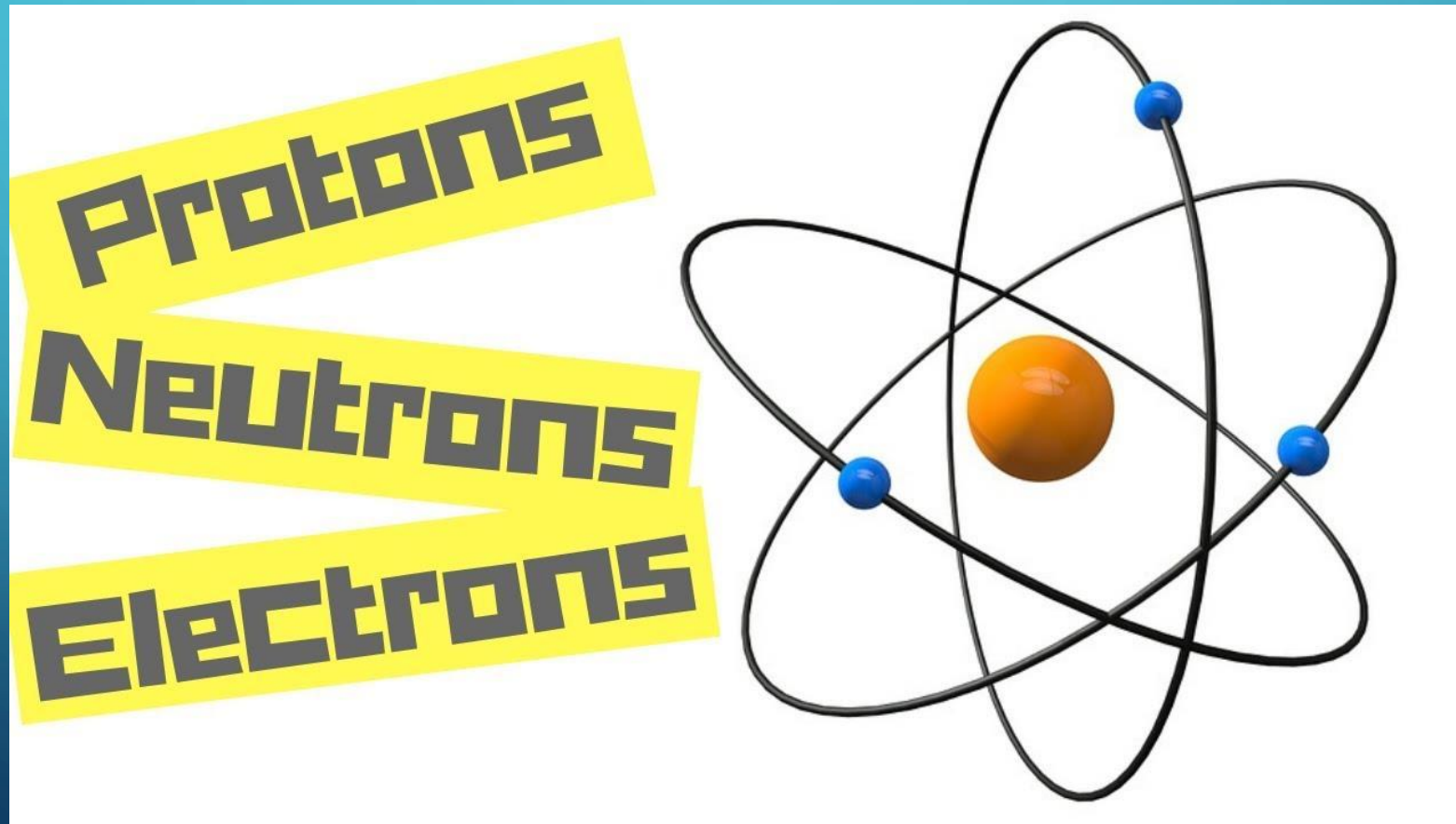


ATOMS

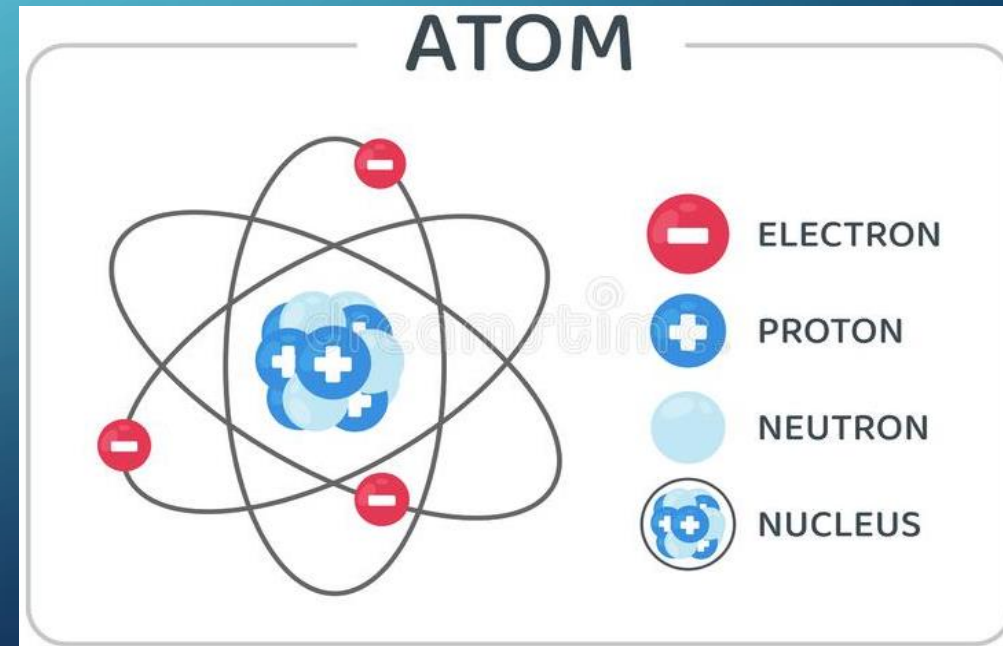- An **atom** is the smallest component of an element and the building blocks of all matter
- An atom consists out of electrons, protons and neutrons
- **Electrons** are negatively charged particles
- **Protons** are positively charged particles
- **Neutrons** are particles without a charge




WHAT IS ELECTRONICS?

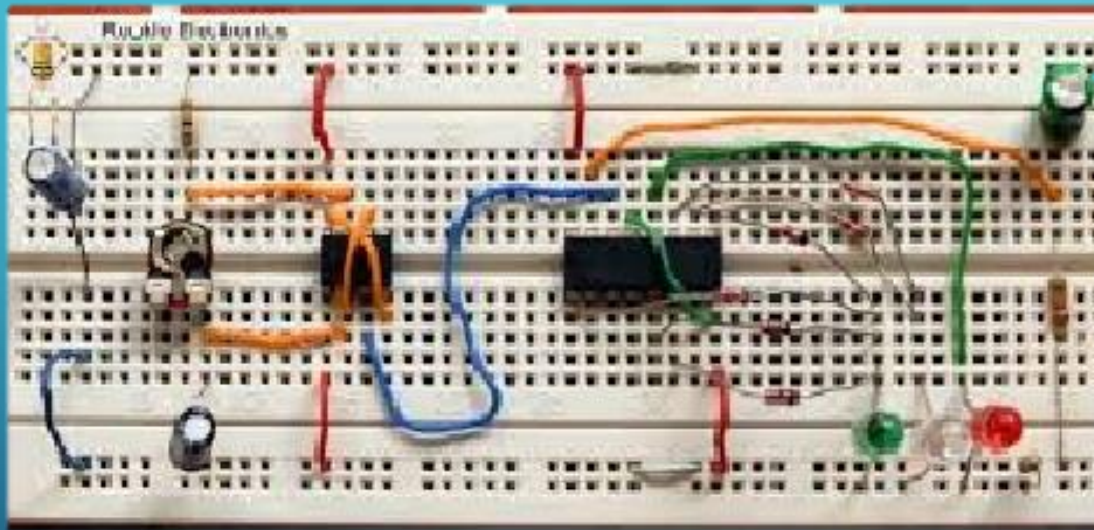

ELECTRONICS

- **Electronics** is in the study and control of electric current
- It controls the quantity and direction of electric current movement as needed
- Electricity and electronics are interrelated in the creation of various electrical appliances
- In an electrical appliance we have an **electrical circuit** that consists out of connected electrical equipment
- Each circuit works in a different way, depending on its functions

WHAT IS AN ELECTRIC CIRCUIT?

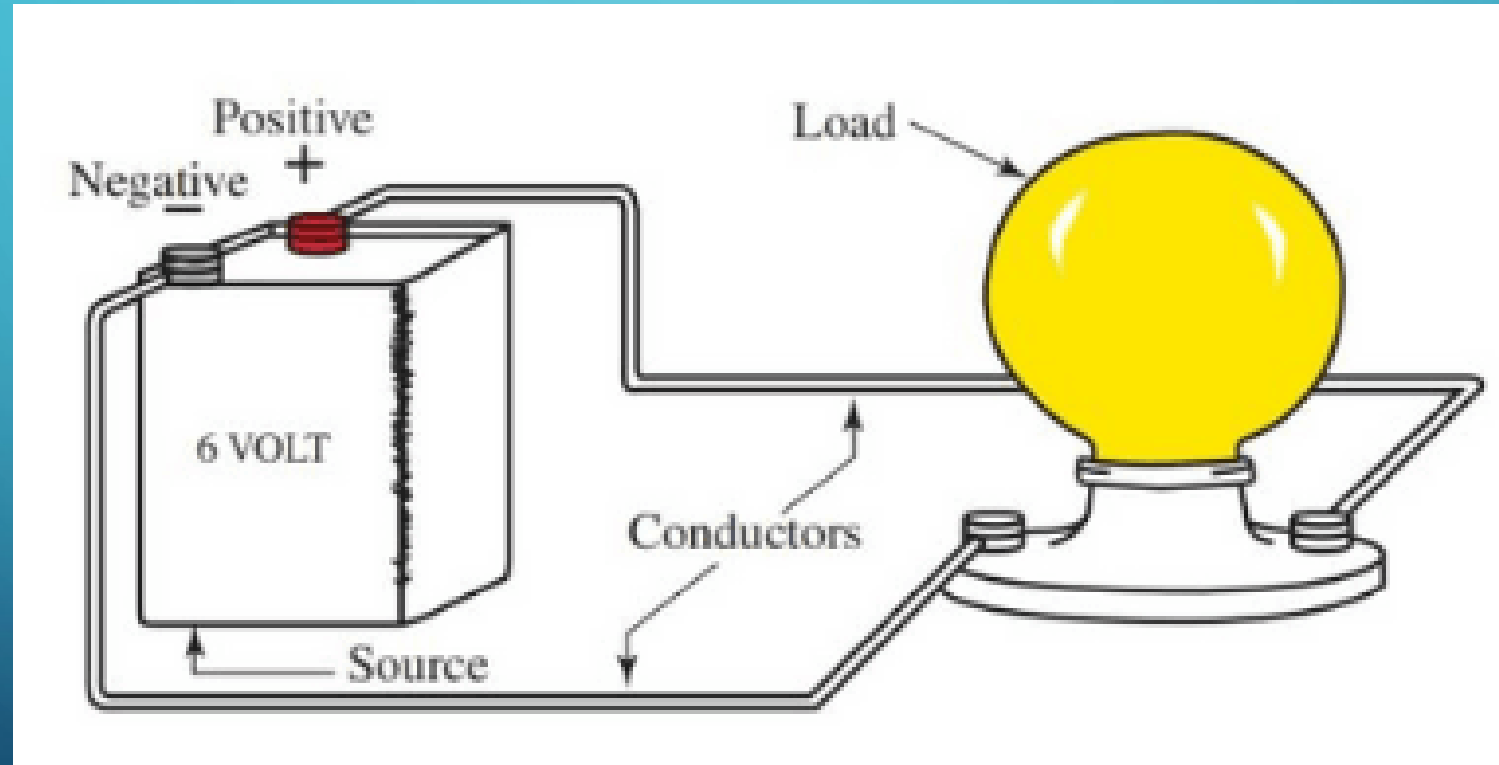


ELECTRIC CIRCUIT

- An **electric circuit** is the conductive path for flow of current or electricity
- An electric circuit has:
 - Device that gives electrical energy (a battery or a generator)
 - Devices that use electrical energy (lamps, electric motors, or computers)
 - Connecting wires or transmission lines



ELECTRIC CIRCUIT

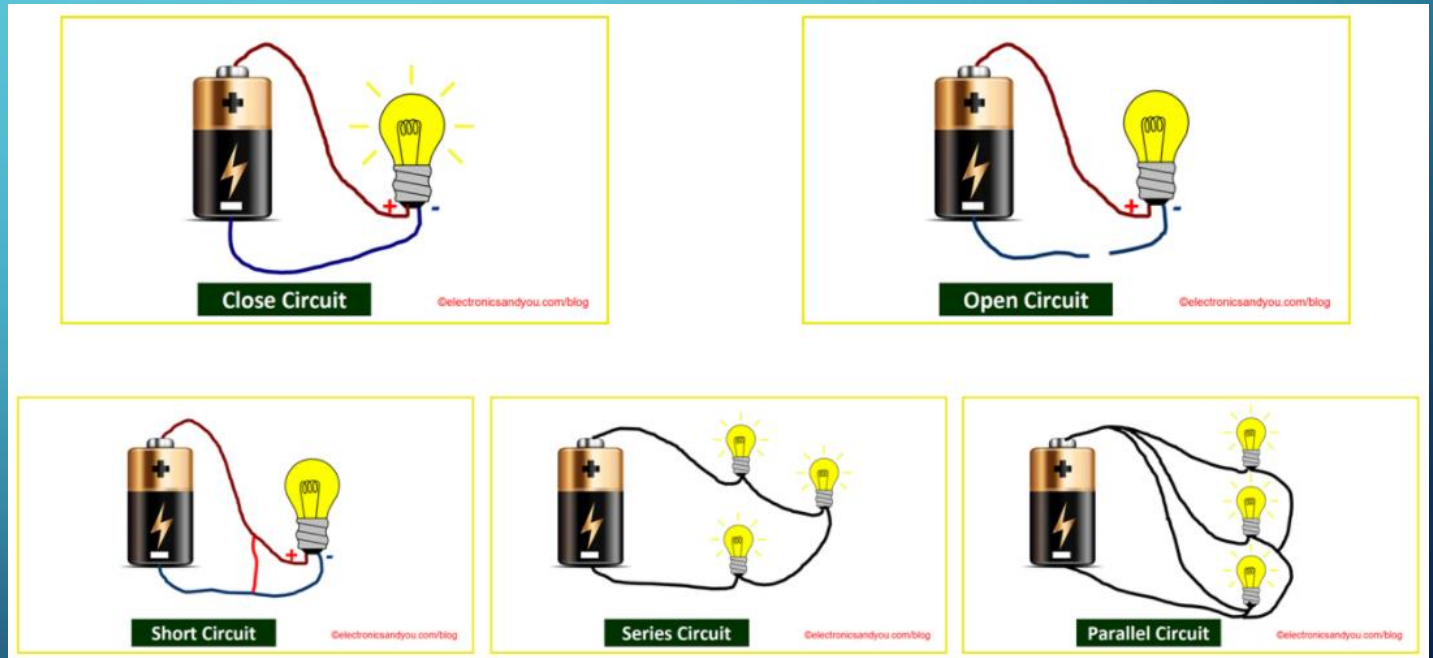- There are 5 main types of electric circuits:
 - Closed Circuit
 - Open Circuit
 - Short Circuit
 - Series Circuit
 - Parallel Circuit





CLOSED CIRCUIT

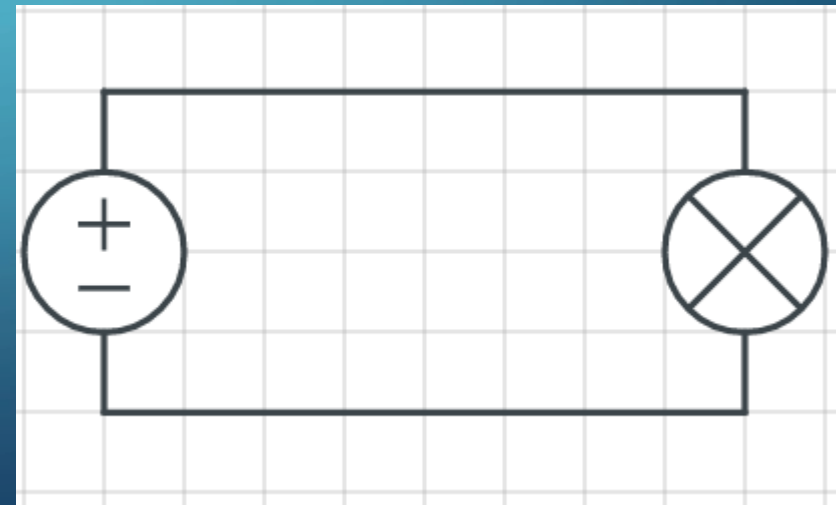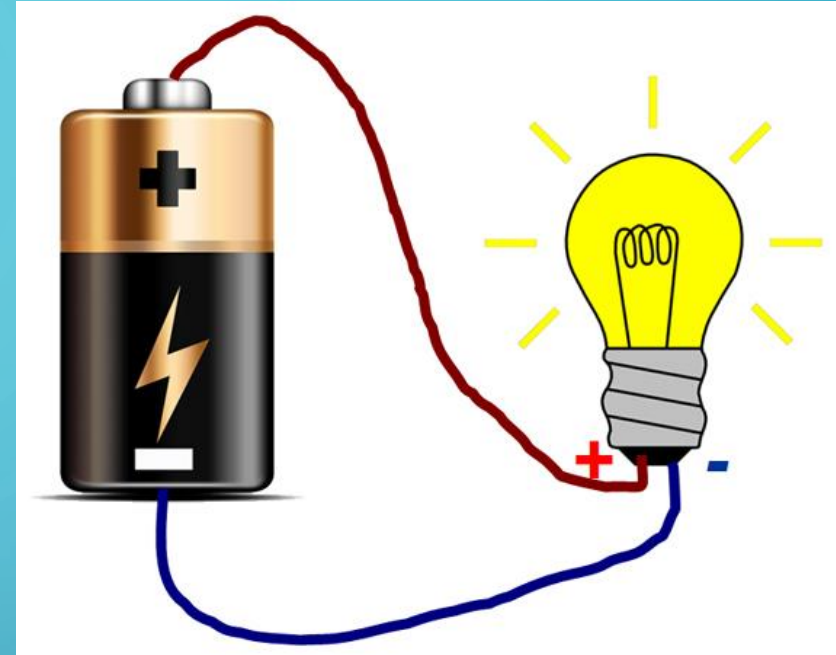- A circuit without interruption
- The circuit is ON
- Electricity flows from one end of the circuit to the other end





OPEN CIRCUIT

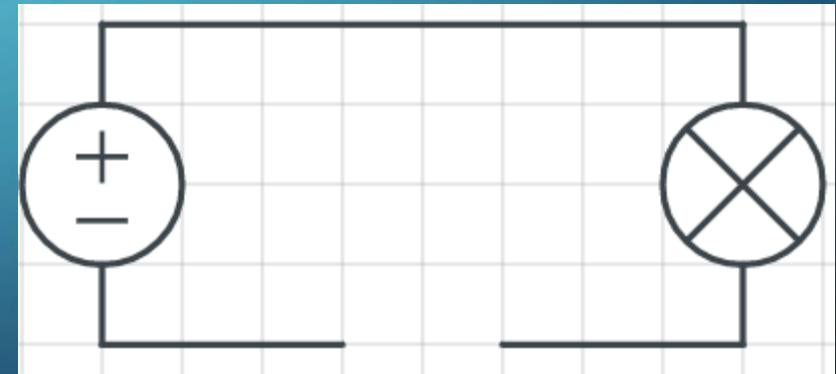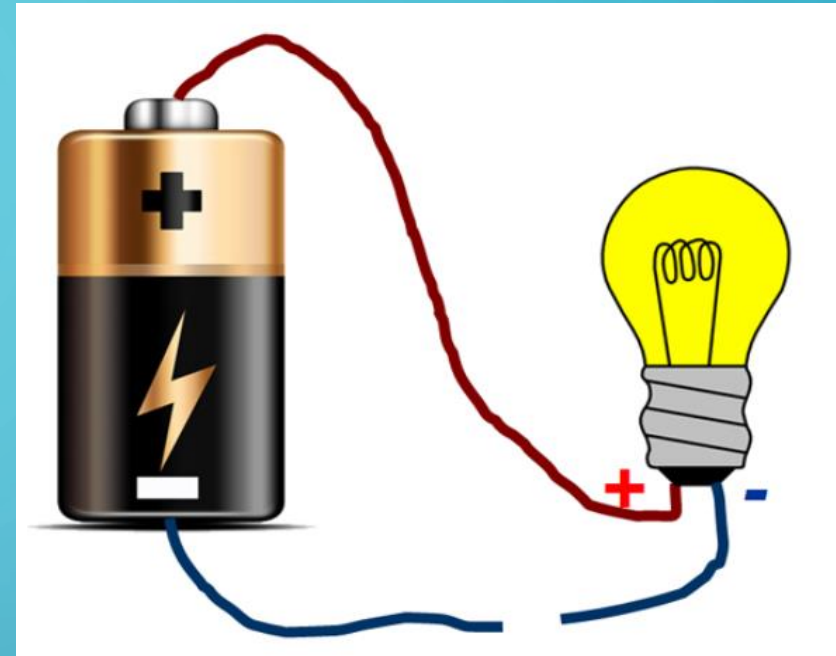- A circuit with interruption
- The circuit is OFF
- Electricity can not flow from one end of the circuit to the other end
- Reasons are either broken wires or the switch is set to off position





SHORT CIRCUIT

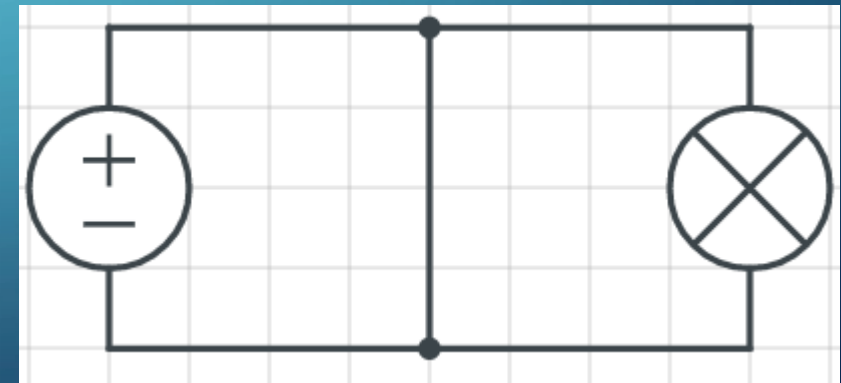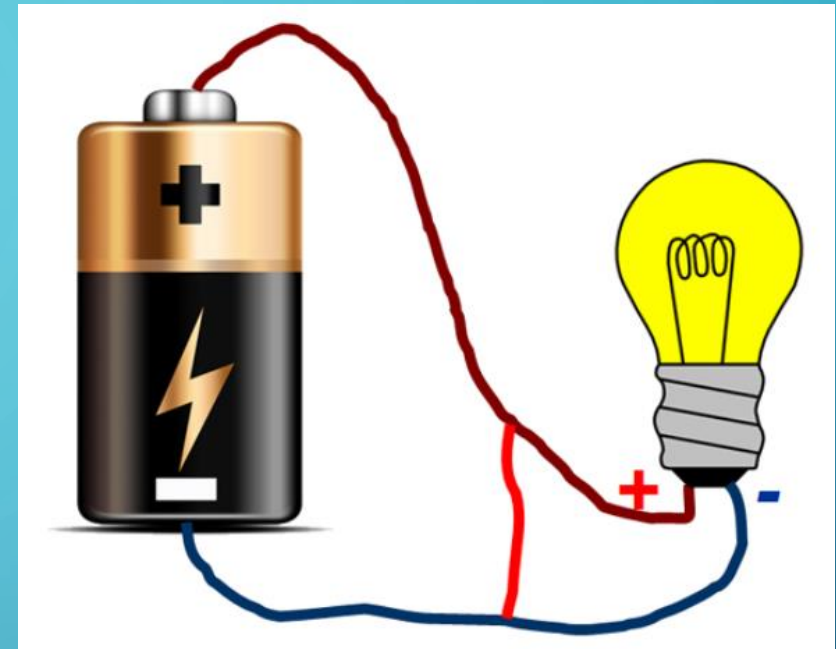- When both points (+ & -) of voltage source in a circuit gets connected with each other for some reason then it is called Short Circuit
- Maximum current starts to flow under this situation





SERIES CIRCUIT

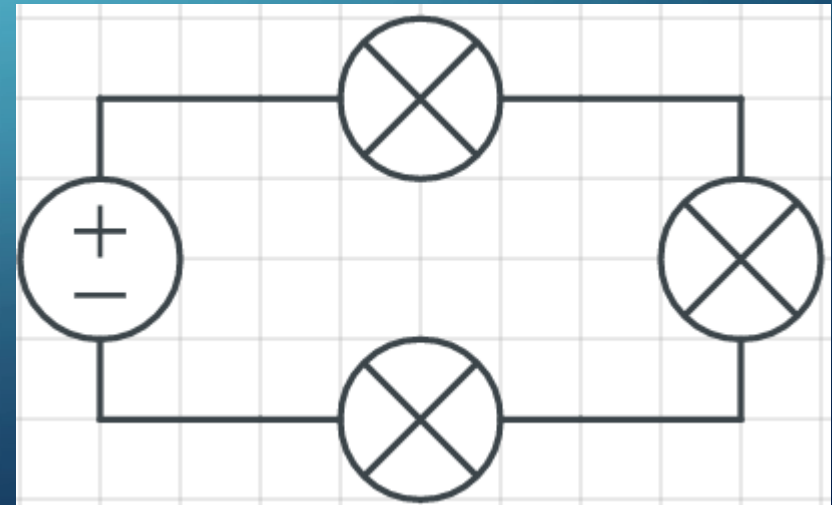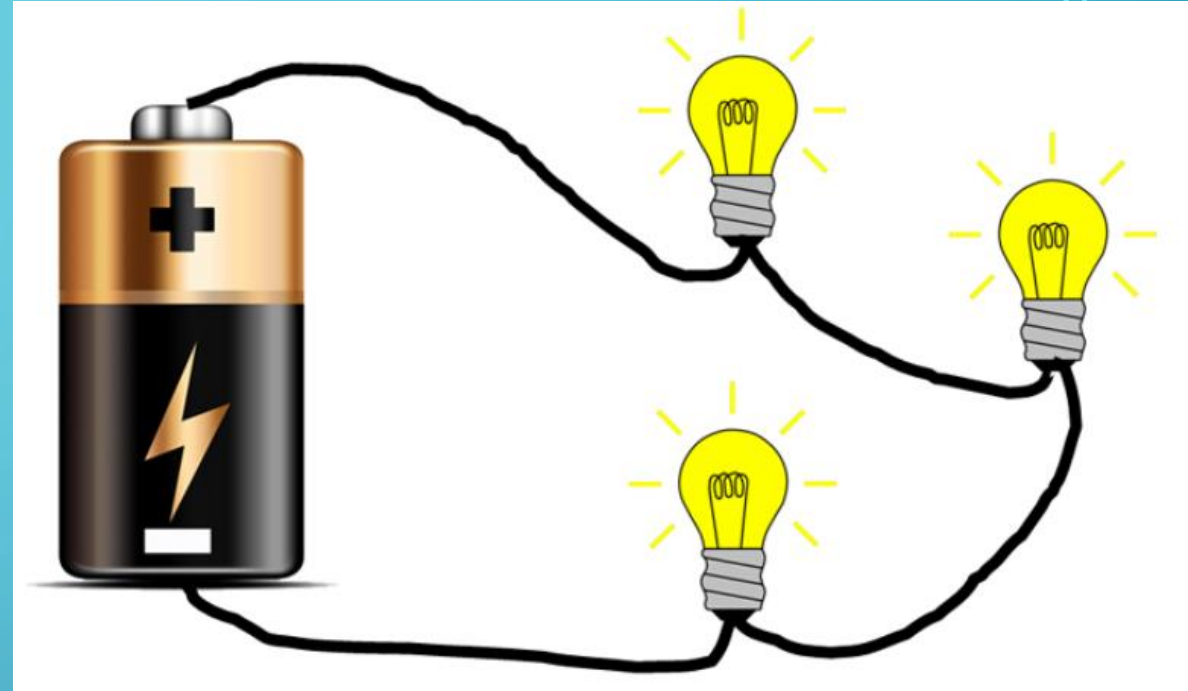- When 2 or more loads (Bulb, CFL, LED, Fan...) are connected to each other in a series
- If one load or bulb stops working, then rest of the bulbs will not get power supply and will not glow




PARALLEL CIRCUIT

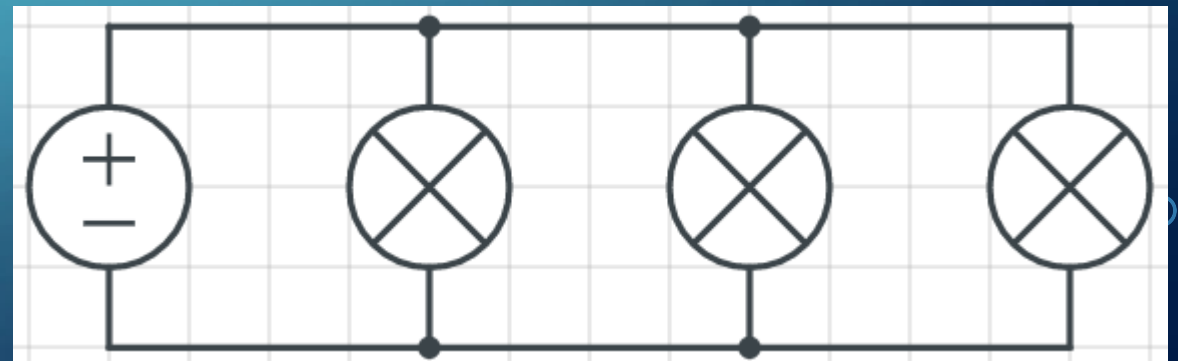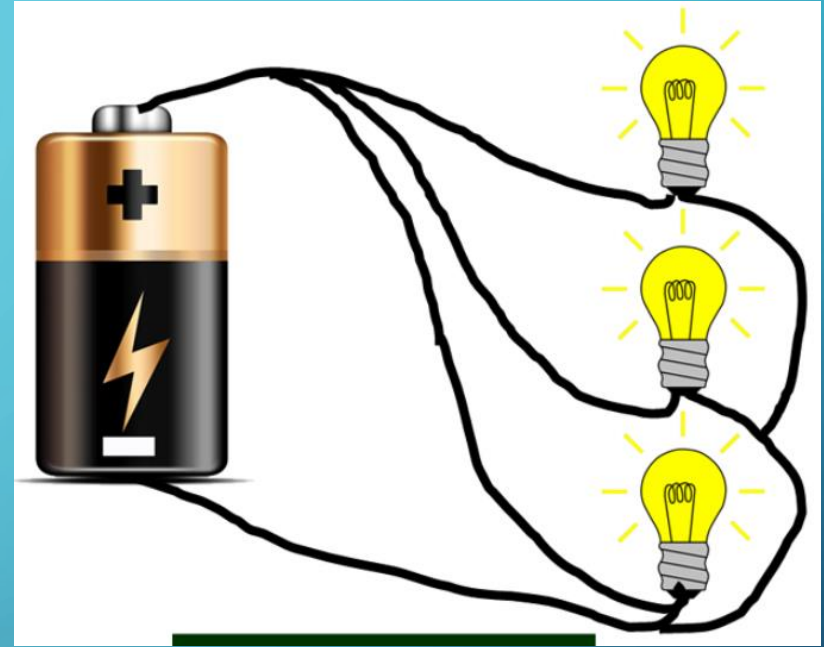- When 2 or more loads (Bulb, CFL, LED, Fan...) are connected to each other in parallel
- If one load or bulb stops working, then rest of the bulbs will still get power supply and will glow




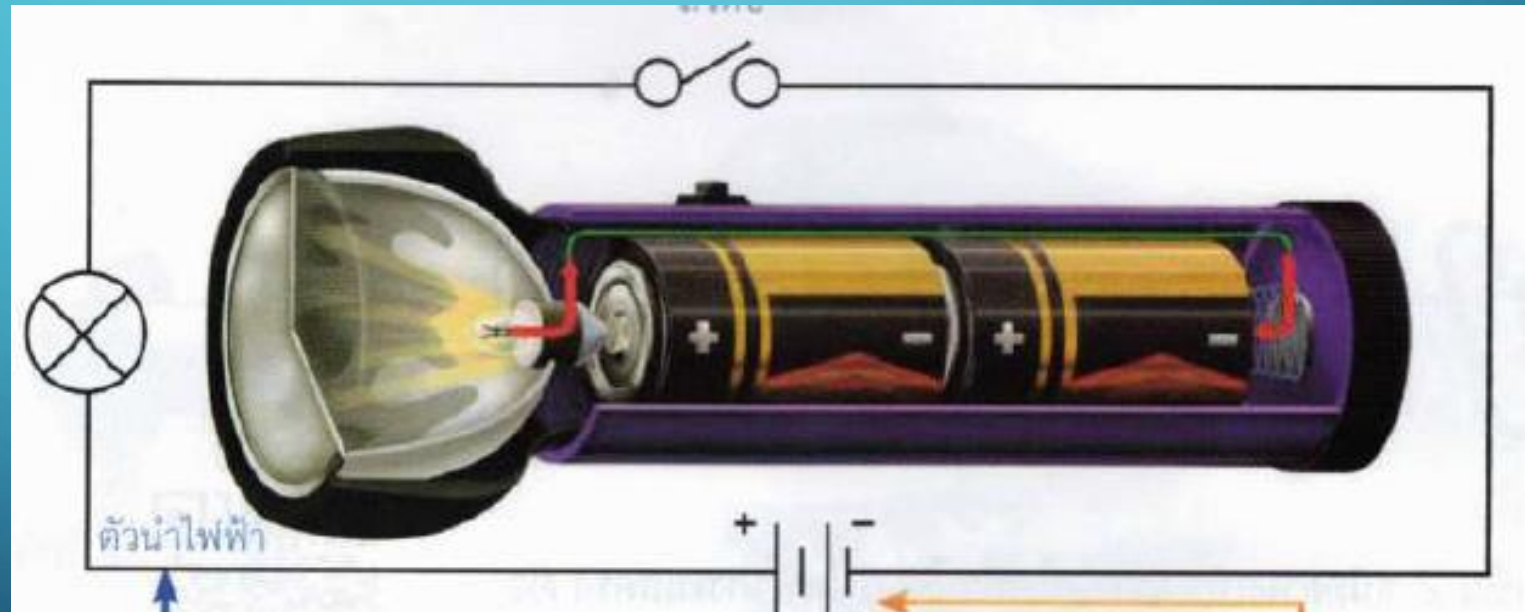EXAMPLE: FLASHLIGHT

- A flashlight can be seen as a simple electrical circuit. It has 3 components,
 - Source
 - Switch
 - Lightbulb



WHAT KIND OF CIRCUIT IS IT?

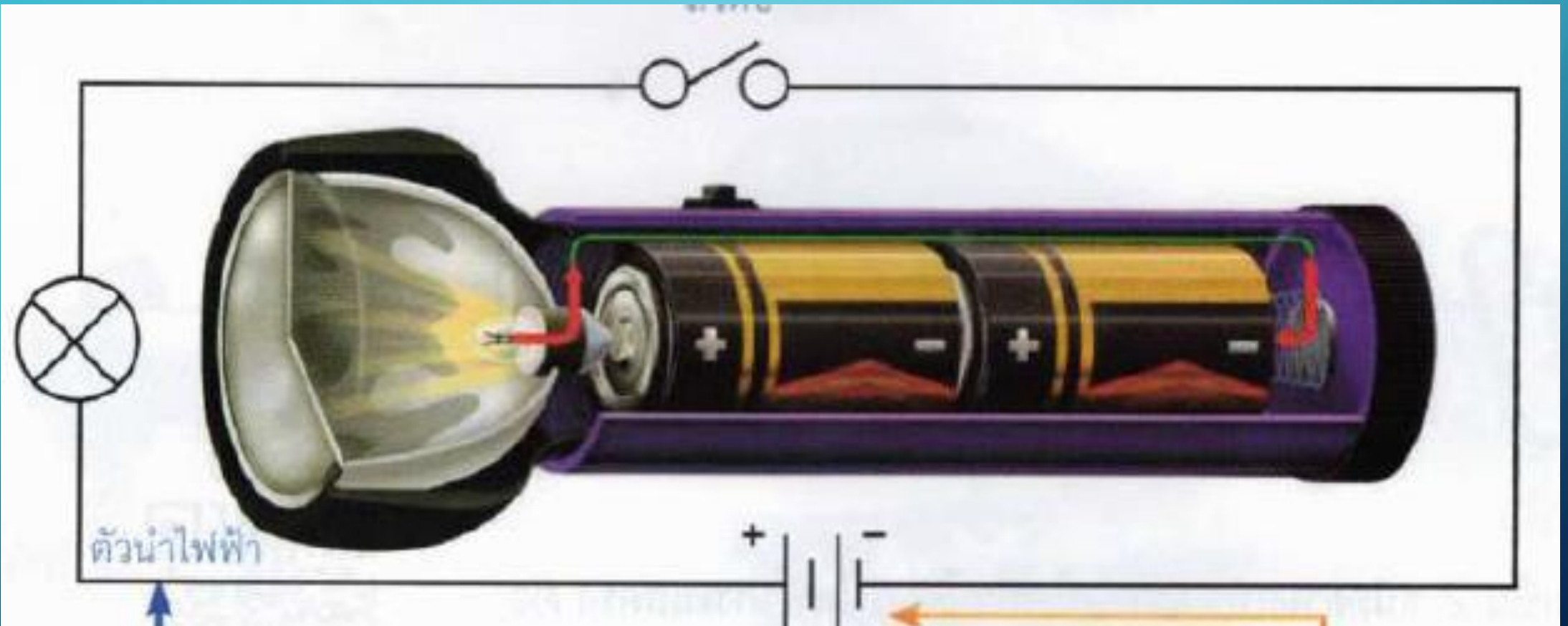



ANY QUESTIONS?



WORKSHEET



THE END